

## ARRL Periodicals Archive – Search Results A membership benefit of ARRL and the ARRL Technical Information Service

**ARRL Members:** You may print a copy for personal use. Any other use of the information requires permission (see Copyright/Reprint Notice below).

**Need a higher quality reprint or scan?** Some of the scans contained within the periodical archive were produced with older imaging technology. If you require a higher quality reprint or scan, please contact the ARRL Technical Information Service for assistance. Photocopies are \$3 for ARRL members, \$5 for nonmembers. For members, TIS can send the photocopies immediately and include an invoice. Nonmembers must prepay. Details are available at www.arrl.org/tis or email photocopy@arrl.org.

**QST on CD-ROM**: Annual CD-ROMs are available for recent publication years. For details and ordering information, visit www.arrl.org/qst.

**Non-Members:** Get access to the ARRL Periodicals Archive when you join ARRL today at www.arrl.org/join. For a complete list of membership benefits, visit www.arrl.org/benefits.


## **Copyright/Reprint Notice**

In general, all ARRL content is copyrighted. ARRL articles, pages, or documents-printed and online--are not in the public domain. Therefore, they may not be freely distributed or copied. Additionally, no part of this document may be copied, sold to third parties, or otherwise commercially exploited without the explicit prior written consent of ARRL. You cannot post this document to a Web site or otherwise distribute it to others through any electronic medium.

For permission to quote or reprint material from ARRL, send a request including the issue date, a description of the material requested, and a description of where you intend to use the reprinted material to the ARRL Editorial & Production Department: permission@arrl.org.

QST Issue: Aug 1960 Title: 813s in Grounded-Grid Author: W.R. Stangel, W6FLT

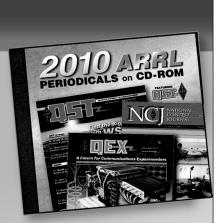Click Here to Report a Problem with this File



# 2010 ARRL Periodicals on CD-ROM

ARRL's popular journals are available on a compact, fullysearchable CD-ROM. Every word and photo published throughout 2010 is included!

- QST The official membership journal of ARRL
- NCJ National Contest Journal
- QEX Forum for Communications Experimenters

SEARCH the full text of every article by entering titles, call signs, names—almost any word. SEE every word, photo (including color images), drawing and table in technical and general-interest features, columns and product reviews, plus all advertisements. **PRINT** what you see, or copy it into other applications.

System Requirements: Microsoft Windows<sup>™</sup> and Macintosh systems, using the industry standard Adobe<sup>®</sup> Acrobat<sup>®</sup> Reader<sup>®</sup> software. The Acrobat Reader is a free download at www.adobe.com.

## 2010 ARRL Periodicals on CD-ROM


ARRL Order No. 2001 Only **\$24.95**\*

\*plus shipping and handling
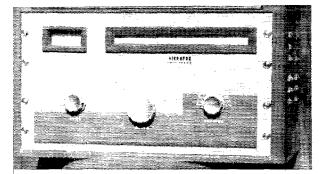
## Additional sets available:

2009 Ed., ARRL Order No. 1486, \$24.95 2008 Ed., ARRL Order No. 9406, \$24.95 2007 Ed., ARRL Order No. 1204, \$19.95 2006 Ed., ARRL Order No. 9841, \$19.95 2005 Ed., ARRL Order No. 9574, \$19.95 2004 Ed., ARRL Order No. 9396, \$19.95 2003 Ed., ARRL Order No. 9124, \$19.95 2002 Ed., ARRL Order No. 8802, \$19.95 2001 Ed., ARRL Order No. 8632, \$19.95





The panel of W6FLT's kilowatt grounded-grid 813 amplifier is designed to match the Apache transmitter which is used as the driver. Controls from left to right are for the band switch, plate tank capacitor and loading capacitor.

BY W. R. STANGEL,\* W6FLT

# Kw. Amplifier for the DX Bands 813s in Grounded-Grid

Over the past several months we have had numerous requests for information on a grounded-grid amplifier using the popular type 813. We are pleased to present this nicely turned out version by W6FLT.

Tany transmitter of the 100-watt-output class serving as the driver. In my own case, the driver happens to be the Heath Apache, thus the similarity in panels. The amplifier operates at 400 ma. and 2250 volts. The total power input to all stages feeding power to the antenna (this includes the final stage of the driver) is one kilowatt. Since my interest lies in only the higher-frequency bands, the design has been confined to the 14-, 21- and 28-Mc. bands. Thus far, the amplifier has been used on c.w. only, but it should be equally satisfactory as an s.s.b. linear when suitably adjusted for this type of operation.

With a low-pass filter and antenna coupler, there is no TVI, even though the TV antenna is almost directly under the 14-Mc. beam. This has not been the case with any grounded-cathode transmitter that has been used previously at this station, which is located in a fringe area.

#### Circuit

The circuit, shown in Fig. 1, is quite conventional for a grounded-grid amplifier. The control grids are not grounded directly, but are suitably bypassed instead to permit the use of grid-leak bias. The screens are grounded directly, placing them in parallel with the control grids so far as r.f. is concerned. The filaments are isolated from ground for r.f. by the bifilar choke  $RFC_1$ . The tank coil in the pi-network output circuit is tapped for the three bands. A.c. and plate-voltage leads are filtered for v.h.f. A fan provides circulation of air around the 813s.

#### Construction

The chassis measures 12 by 17 by 2 inches and is spaced 1¼ inches behind the  $10\frac{1}{2} \times 19$ -inch panel to allow room for the dial assembly, bandswitch drive and dial lamps. The shielding enclosure is 12 by 13 by 8¼ inches, leaving a 4-inch space at the left-hand end of the chassis for the filament and dial-lamp transformers. The back and sides of the enclosure are made of Reynolds perforated aluminum sheet. The right-hand end and back are extended so that they may be fastened to the apron surfaces of the chassis. The bottom edge of the remaining side is bent over to form a lip by which this side may be secured to the surface of the chassis. The front edges of the two sides of the box also have lips for fastening to the front wall. The latter is a sheet of solid aluminum attached to the front apron of the chassis. The cover is secured by a series of 4-36 machine screws tapped into 14-inch square brass rod running around the top edge of the enclosure. Screw holes are spaced 2 inches apart.

The placement of components within the shielding compartment may be determined from the top-view photograph. The tank capacitor is mounted directly on the chassis and is placed so that its shaft is central in respect to the panel (not the front wall of the enclosure). The tank coil and band switch are mounted close to the capacitor. A separate coil section is used for 10 meters, as indicated in Fig. 1. The switch is driven by the left-hand panel knob by means of a metal band and a pair of pulleys. The band is made from 14-inch shim stock obtained from an automobile supply store. The pulleys are  $1\frac{1}{2}$ inches in diameter and the band is pinned to the pulleys to keep it from slipping. The switch was taken from a BC-375 tuning unit but I have had no trouble with an ordinary receiving-type ceramic switch which I used in another amplifier running at 800 watts input. Copper braid, 14-inch wide, is used for the coil tap leads.

The shaft of the pi-network output capacitor, mounted to the right, runs within an inch or so of the tank coil, so a section of insulated rod was

40

<sup>\*</sup>P. O. Box 392. Lakeport, California.

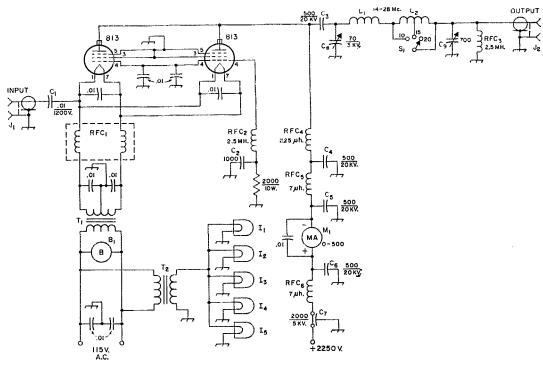


Fig. 1—Circuit of the 813 grounded-grid amplifier. Capacitances less than 0.01  $\mu$ f. are in  $\mu\mu$ f. Capacitors not listed below are disc ceramic.

B<sub>1</sub>-Fan and motor (Elmar Electronics\*).

C1-Mica.

- C<sub>2</sub>-500-volt disk ceramic.
- C3, C4, C5, C6-TV "Doorknob" ceramic.
- C7-Feed-through type (Sprague 47P16).
- Cs-3000-volt variable (Johnson 155-9).
- C<sub>9</sub>—Dual b.c. replacement-type variable, 350  $\mu\mu$ f. per section, sections in parallel.
- I<sub>1</sub>-I<sub>5</sub> inc.—6.3-volt dial lamp.
- J<sub>1</sub>, J<sub>2</sub>—Chassis-mounting coax receptacle (SO-239).
- L1-3 turns 1/2-inch copper strap, 1-inch diam., 13/4 inches long.

inserted between the capacitor shaft and the panel control shaft.

The sockets of the 813s are submounted flush against the under side of the chassis with Pins 3 and 5 grounded to the nearest mounting screws. The filament choke is mounted close to the sockets and the capacitors shunting the filaments are connected directly at the socket terminals. Bypasses are grounded at the nearest point on the chassis. The hardware was removed from the R-175-A choke and the unit mounted directly on the chassis. The fan is mounted on rubber shock mounts to reduce noise and vibration.

The r.f. input connector is set in the rear edge of the chassis at the closest point to the tube sockets. The output connector is mounted above chassis in the rear wall of the enclosure at a point close to the loading capacitor. A Millen safety terminal is used for the high-voltage connection and a barrier strip for the a.c. connections. Highvoltage test-lead wire covered with copper braid

\*140 11th St., Oakland 7, Calif.

. . . . . . . . . . . .

## **August 1960**


- L<sub>2</sub>—9 turns  $\frac{1}{4}$ -inch copper tubing, 2 $\frac{1}{4}$ -inch diam., 4 inches long, tapped at 21/2 and 6 turns from output end.
- M1-D.c. milliammeter.
- RFC1-Barker & Williamson FC-15. RFC<sub>2</sub>-125-ma, r.f. choke (National R-100S).
- RFC<sub>3</sub>-50 ma. r.f. choke. RFC4-National R-175-A.
- RFC5, RFC6-V.h.f. choke (Ohmite Z-50).
- S1-See text.
- -10-volt 10-amp. filament transformer (Merit P-3146, T<sub>1</sub>-Stancor P-6461 or similar).
- T2--6.3-volt 1-amp. filament transformer (Thordarson 21F08).

is used for the high-voltage wiring. Connections between the top of the plate r.f. choke and the plates of the 813s are made with  $\frac{1}{2}$ -inch copper braid.

The shaft of the tank capacitor extends through to the center knob on the panel. This shaft carries a 5<sup>1</sup>/<sub>4</sub>-inch dial pullev mounted between the panel and the shielding enclosure. The dial scale is drawn on white paper and then glued to a plate of  $\frac{1}{16}$ -inch aluminum measuring  $2\frac{1}{2}$  by 11 inches. The plate is mounted on the front of the shielding enclosure on 34-inch spacers. A small pulley is mounted at each end of the plate and the dial cable runs from the large pulley on the tank-capacitor shaft over and across the small pulleys and back to the drive pulley. The pointer, salvaged from an old radio receiver, is fastened to the dial cable. The diameter of the drive pulley restricts the movement of the pointer to less than the full dial length, so the 0 and 100 points on the scale are a distance from the ends of the dial plate. The escutcheons, control knobs

------

41

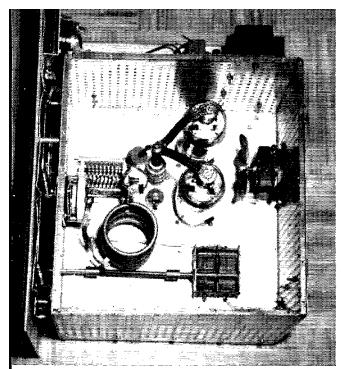

and a meter-mounting bracket were obtained from Heath as replacement parts. The panel decoration is a strip of 1/2-inch Masonite cut to match the one on the Apache.

The meter is in the high-voltage lead to the plate and therefore the meter should be recessed and insulated from its mounting. The meter was insulated from the metal mounting bracket by applying empire cloth, holding it in place with plastic tape.

The dial scale is illuminated by three dial lamps, one in the center and one at each end; two lamps illuminate the meter.

#### Adjustment

The tuning procedure to be used with a grounded-grid amplifier differs from that usually followed in adjusting a grounded-cathode stage. Some form of output indicator is a necessity. Although a point will be found where the plate eurrent dips with tuning of the output tank circuit, this may not, and probably will not, be the point of maximum output.

Also, the output will be found to vary widely with the driving power applied. I use my standing-wave indicator set in the "forward" position as an output indicator. Alternatively, a fieldstrength meter will serve.

The length of the coax between the output of the driver and the input of the amplifier should be kept as short as practicable, since the input impedance of the amplifier changes considerably with drive and loading adjustments, making it virtually impossible to maintain a proper termination for the coax line.

It is advisable to reduce plate voltage during the initial tune-up procedure, although the plate power input can be held to a safe value by keeping Interior view of the 813 grounded-grid amplifier.

the driving input down. Plate voltage on the amplifier should be turned off while the driver is first adjusted to resonance with its output coupling reduced to minimum. Set the amplifier tank capacitor at about half maximum capacitance and the output capacitor at about  $\frac{2}{3}$  maximum

(assuming a 50-ohm load). Now apply plate voltage to the amplifier. The idling current at 2500 volts, and without excitation should be about 70 ma. Increase the coupling to the driver until the amplifier plate current increases to 150 or 200 ma. Adjust both tank and loading capacitors for maximum output. These controls interlock, requiring a process of juggling until the maximumoutput settings are found. Now the driver coupling can be increased until the input to the driver is at maximum rating (assuming a driver in the 100-watt-or-so-output class). Simultaneously, the loading of the amplifier should be readjusted so that the sum of the inputs to the driver and the amplifier does not exceed 1000 watts. With the Apache loaded to an input of 180 watts, the grid current to the amplifier runs about 40 ma. and the voltage across the grid leak is 80 volts. Using the standard methods of checking, no tendency toward parasitic oscillation was found and no other difficulties have been met in operating the amplifier on any of the three bands. Q57-

### Strays S

When a new man arrives at Fort Carson, Colo., his parents learn of his safe arrival promptly, thanks to members of the Springs-Peak Amateur Radio Club working through the MARS station.

Among the sheaf of papers handed to new arrivals is a slip on which they can write messages for the tolks at home. The messages are collected every morning. Military officials have praised the system as a morale-builder for the men and their families. The idea came from Capt. Eric Hogberg, a charter member of the amateur radio club at Carson.

QST for

42