



## ARRL Periodicals Archive – Search Results

### A membership benefit of ARRL and the ARRL Technical Information Service

**ARRL Members:** You may print a copy for personal use. Any other use of the information requires permission (see Copyright/Reprint Notice below).

**Need a higher quality reprint or scan?** Some of the scans contained within the periodical archive were produced with older imaging technology. If you require a higher quality reprint or scan, please contact the ARRL Technical Information Service for assistance. Photocopies are \$3 for ARRL members, \$5 for nonmembers. For members, TIS can send the photocopies immediately and include an invoice. Nonmembers must prepay. Details are available at [www.arrl.org/tis](http://www.arrl.org/tis) or email [photocopy@arrl.org](mailto:photocopy@arrl.org).

**QST on CD-ROM:** Annual CD-ROMs are available for recent publication years. For details and ordering information, visit [www.arrl.org/qst](http://www.arrl.org/qst).

**Non-Members:** Get access to the ARRL Periodicals Archive when you join ARRL today at [www.arrl.org/join](http://www.arrl.org/join). For a complete list of membership benefits, visit [www.arrl.org/benefits](http://www.arrl.org/benefits).

### Copyright/Reprint Notice

In general, all ARRL content is copyrighted. ARRL articles, pages, or documents--printed and online--are not in the public domain. Therefore, they may not be freely distributed or copied. Additionally, no part of this document may be copied, sold to third parties, or otherwise commercially exploited without the explicit prior written consent of ARRL. You cannot post this document to a Web site or otherwise distribute it to others through any electronic medium.


For permission to quote or reprint material from ARRL, send a request including the issue date, a description of the material requested, and a description of where you intend to use the reprinted material to the ARRL Editorial & Production Department: [permission@arrl.org](mailto:permission@arrl.org).

**QST Issue:** Mar 1969

**Title:** Amplifying Low-Level VFO Output

**Author:** Doug DeMaw, W1CER

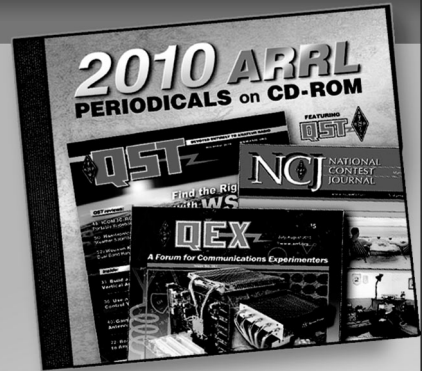[Click Here to Report a Problem with this File](#)



## 2010 ARRL Periodicals on CD-ROM

ARRL's popular journals are available on a compact, fully-searchable CD-ROM. Every word and photo published throughout 2010 is included!

- **QST** The official membership journal of ARRL
- **NCJ** National Contest Journal
- **QEX** Forum for Communications Experimenters

**SEARCH** the full text of every article by entering titles, call signs, names—almost any word. **SEE** every word, photo (including color images), drawing and table in technical and general-interest features, columns and product reviews, plus all advertisements. **PRINT** what you see, or copy it into other applications.

**System Requirements:** Microsoft Windows™ and Macintosh systems, using the industry standard Adobe® Acrobat® Reader® software. The Acrobat Reader is a free download at [www.adobe.com](http://www.adobe.com).

### 2010 ARRL Periodicals on CD-ROM

ARRL Order No. 2001

**Only \$24.95\***

\*plus shipping and handling

Additional sets available:

2009 Ed., ARRL Order No. 1486, \$24.95  
 2008 Ed., ARRL Order No. 9406, \$24.95  
 2007 Ed., ARRL Order No. 1204, \$19.95  
 2006 Ed., ARRL Order No. 9841, \$19.95  
 2005 Ed., ARRL Order No. 9574, \$19.95  
 2004 Ed., ARRL Order No. 9396, \$19.95  
 2003 Ed., ARRL Order No. 9124, \$19.95  
 2002 Ed., ARRL Order No. 8802, \$19.95  
 2001 Ed., ARRL Order No. 8632, \$19.95



**ARRL** The national association for AMATEUR RADIO™

SHOP DIRECT or call for a dealer near you.  
 ONLINE [WWW.ARRL.ORG/SHOP](http://WWW.ARRL.ORG/SHOP)  
 ORDER TOLL-FREE 888/277-5289 (US)



# Hints and Kinks

For the Experimenter



## USING A LEFTOVER ROTATOR-TO-MAST FLANGE AS AN ANTENNA-TO-MAST BRACKET

THE leftover rotator-to-mast flange, CDR part TRA-2, which is not used if an AR-22 or TR-44 series rotator is bolted to a flat plate, as in an in-tower mounting, may be pressed into service as an antenna-to-mast bracket by securing the boom to the flat side of the flange and clamping the flange to the antenna mast. — *Bob Wheaton, W5PKK*

## EQUALLY SPACING PANEL CONTROLS

TO lay out a panel so that any number of controls may be equally spaced, let  $X$  equal the desired number of controls. Then, as shown in Fig. 1, place a ruler along the lower edge of the panel and slant the right-hand end of the ruler upward until the edge of the panel intersects  $X + 1$  divisions on the ruler. Draw a line along the ruler and mark off the divisions. Using a T square, complete the job by drawing a line perpendicular to the bottom of the panel through each division. — *Melvin Leibowitz, W3KET*

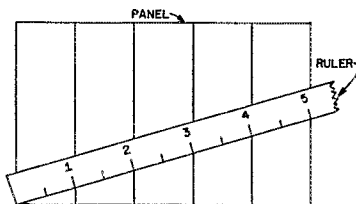


Fig. 1—Slanting a ruler on a panel makes it easy to equally space any number of controls.

## CLEANING THE HEAD OF A SPRAY PAINT CAN

WHEN using a spray can of paint one has to clean the spray head between jobs so that paint won't harden in the head and block the passage. This cleaning is usually done by turning the can upside down and spraying until the nozzle is empty of paint or by removing the spray head and cleaning it by hand with paint or lacquer thinner and a fine wire. The first method is wasteful, and the latter is a messy job at best.

With the use of spray contact cleaner or circuit cooler one can neatly and economically clean the spray heads from spray paint cans. Simply remove the spray head from the cleaner or circuit cooler and substitute the head that is to be cleaned. A couple of squirts of cleaner through the head will clean it thoroughly. — *Lloyd L. Shoman, W0EYS/0*

## ETCH-RESISTANT CIRCLES

EVER have difficulty painting small, nearly perfect etch-resistant circles on copper-clad board? Use a paper punch to punch holes in masking tape and use the tape as a guide. — *Paul Maurice.*

## AMPLIFYING LOW-LEVEL V.F.O. OUTPUT

MOST solid-state v.f.o.'s deliver less than 10 volts peak across their low-impedance output terminals. More often than not the output voltage is only two or three volts.<sup>1,2</sup> If the v.f.o. is to drive a vacuum-tube stage in a transmitter, considerably more voltage swing will be needed at the tube grid in order to obtain satisfactory output from the tube stage. If the driven stage does not consume appreciable power from the v.f.o., the typical circuits shown in Fig. 2 can be used between the low-impedance output of the v.f.o. and the normally high-impedance input of the tube stage. Both circuits shown have given good results when amplifying the 3-volt peak output of a test v.f.o. to a suitable level for driving the oscillator stages of several tube-type transmitters.

In Fig. 2A, the v.f.o. output signal is amplified by a 5-watt n-p-n transistor,  $Q_1$ , which operates Class A.  $L_1$  is a low-impedance winding on the cold end of  $L_2$ , and the combination of the two windings provides a step-up ratio between the transistor output and the vacuum-tube input. The  $Q$  of the output circuit,  $L_2C_1$ , is determined by the  $L/C$  ratio used. Low values of  $C$  will result in lower  $Q$  and greater bandwidth — useful for QSYing. Unfortunately, a low- $C$  circuit will not discriminate well against harmonic currents, so a compromise should be sought. In Table I typical  $L$  and  $C$  values, which should be satis-

<sup>1</sup> "A General-Purpose V.F.O.," *QST*, September, 1968.  
<sup>2</sup> Hanchett, "The Field-Effect Transistor as a Stable V.F.O. Element," *QST*, December, 1966.

Table I  
Tuned Circuit Data

$L_1$  coils are closewound with No. 30 enameled wire at ground end of  $L_2$  coils (Miller).  
 $C_1$  capacitors are ceramic or mica.

Freq. in MHz.	$L_1$ (turns)	$L_2$ (uh.)	$C_1$ (pf.)	Miller No.
1.8 to 2.0	30	138-238	50	4410
3.0 to 4.0	22	74-124	30	4409
5.0 to 6.0	15	33-66	22	4408
6.6 to 7.5	15	33-66	22	4408
7.5 to 9.0	10	16-29	15	4407

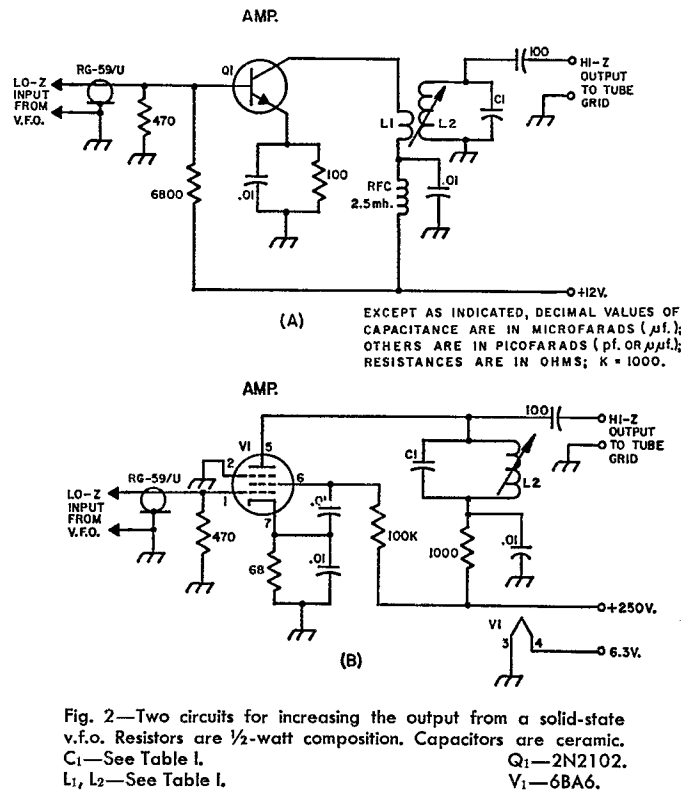


Fig. 2—Two circuits for increasing the output from a solid-state v.f.o. Resistors are 1/2-watt composition. Capacitors are ceramic. C<sub>1</sub>—See Table I. L<sub>1</sub>, L<sub>2</sub>—See Table I.

factory for most applications, are given for some of the popular v.f.o. tuning ranges.

In the circuit of Fig. 2B, a vacuum-tube Class-A amplifier, V<sub>1</sub>, is used between the transistor v.f.o. and the input to a tube stage. The grid circuit of V<sub>1</sub> uses a 470-ohm resistor to afford an impedance match to the v.f.o. output terminals and to load the v.f.o. output circuit to minimize interaction between the amplifier stage and the v.f.o. The signal is taken from the high-impedance end of L<sub>2</sub> and is capacitively coupled to the grid circuit of the stage to be driven. Since the vacuum-tube amplifier does not produce harmonic currents of the magnitude that the circuit of Fig. 2A is capable of generating, it is not important in this instance to strive for a high-Q output tuned circuit for the purpose of harmonic reduction. The higher the Q, however, the greater will be the peak output voltage available from these two circuits.

In the v.f.o. amplifier circuits shown, it's OK to substitute other types of transistors and tubes provided they have electrical characteristics similar to the ones specified in the schematic caption. It is important that the amplifiers be well shielded and bypassed to prevent transmitter r.f. from affecting their performance. The coupling cable (RG-59/U) from the v.f.o. to either of these circuits should be as short as possible, and the v.f.o. amplifier should be located near the stage being driven and preferably on the same chassis. — WICER

### EASY TRANSFORMER MOUNTING

THE cumbersome task of having to saw or file comparatively large rectangular holes for power transformers, chokes and the like can be dispensed with by the use of four spade bolts. As shown in Fig. 3, mount a spade bolt at each end of two of the four existing screws that sandwich together the transformer's laminations and metal cover. Feed the spade bolts through four small holes drilled through the chassis, and then secure the bolts with lock washers and nuts on the underside. Finally, drill a hole for the primary and secondary leads and, of course, fit it with a grommet. — John E. Maass, K7JKZ

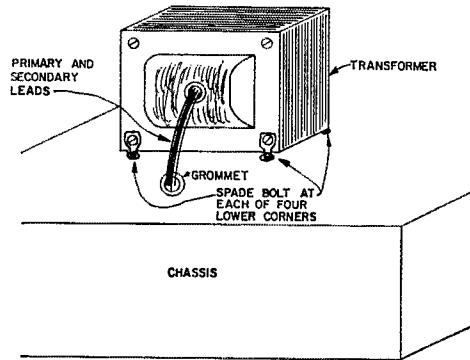


Fig. 3—By mounting a transformer as shown, much chassis work is eliminated.